

A full die photograph of the MIPS R2000 RISC Microprocessor is shown above. The 1986 MIPS R2000 with five pipeline stages and 450,000 transistors was the world's first commercial RISC microprocessor. Photograph ©1995-2004 courtesy of Michael Davidson, Florida State University.

Table 14.1 MIPS 32-bit Instruction Formats.

| Field Size | 6-bits | 5-bits | 5-bits | 5-bits | 5-bits | 6-bits |
|-------------------|---------------|-----------------------|---------------|-------------------------|---------------|---------------|
| R - Format | Opcode | Rs | Rt | Rd | Shift | Function |
| I - Format | Opcode | Rs | Rt | Address/immediate value | | |
| J - Format | Opcode | Branch target address | | | | |

| | |
|-------------------|--|
| LW \$2, B | ;Register 2 = value of memory at address B |
| LW \$3, C | ;Register 3 = value of memory at address C |
| ADD \$4, \$2, \$3 | ;Register 4 = B + C |
| SW \$4, A | ;Value of memory at address A = Register 4 |

Table 14.2 MIPS Processor Core Instructions.

| Mnemonic | Format | Opcode Field | Function Field | Instruction |
|-----------------|---------------|---------------------|-----------------------|---------------------------------|
| Add | R | 0 | 32 | Add |
| Addi | I | 8 | - | Add Immediate |
| Addu | R | 0 | 33 | Add Unsigned |
| Sub | R | 0 | 34 | Subtract |
| Subu | R | 0 | 35 | Subtract Unsigned |
| And | R | 0 | 36 | Bitwise And |
| Or | R | 0 | 37 | Bitwise OR |
| Sll | R | 0 | 0 | Shift Left Logical |
| Srl | R | 0 | 2 | Shift Right Logical |
| Slt | R | 0 | 42 | Set if Less Than |
| Lui | I | 15 | - | Load Upper Immediate |
| Lw | I | 35 | - | Load Word |
| Sw | I | 43 | - | Store Word |
| Beq | I | 4 | - | Branch on Equal |
| Bne | I | 5 | - | Branch on Not Equal |
| J | J | 2 | - | Jump |
| Jal | J | 3 | - | Jump and Link (used for Call) |
| Jr | R | 0 | 8 | Jump Register (used for Return) |

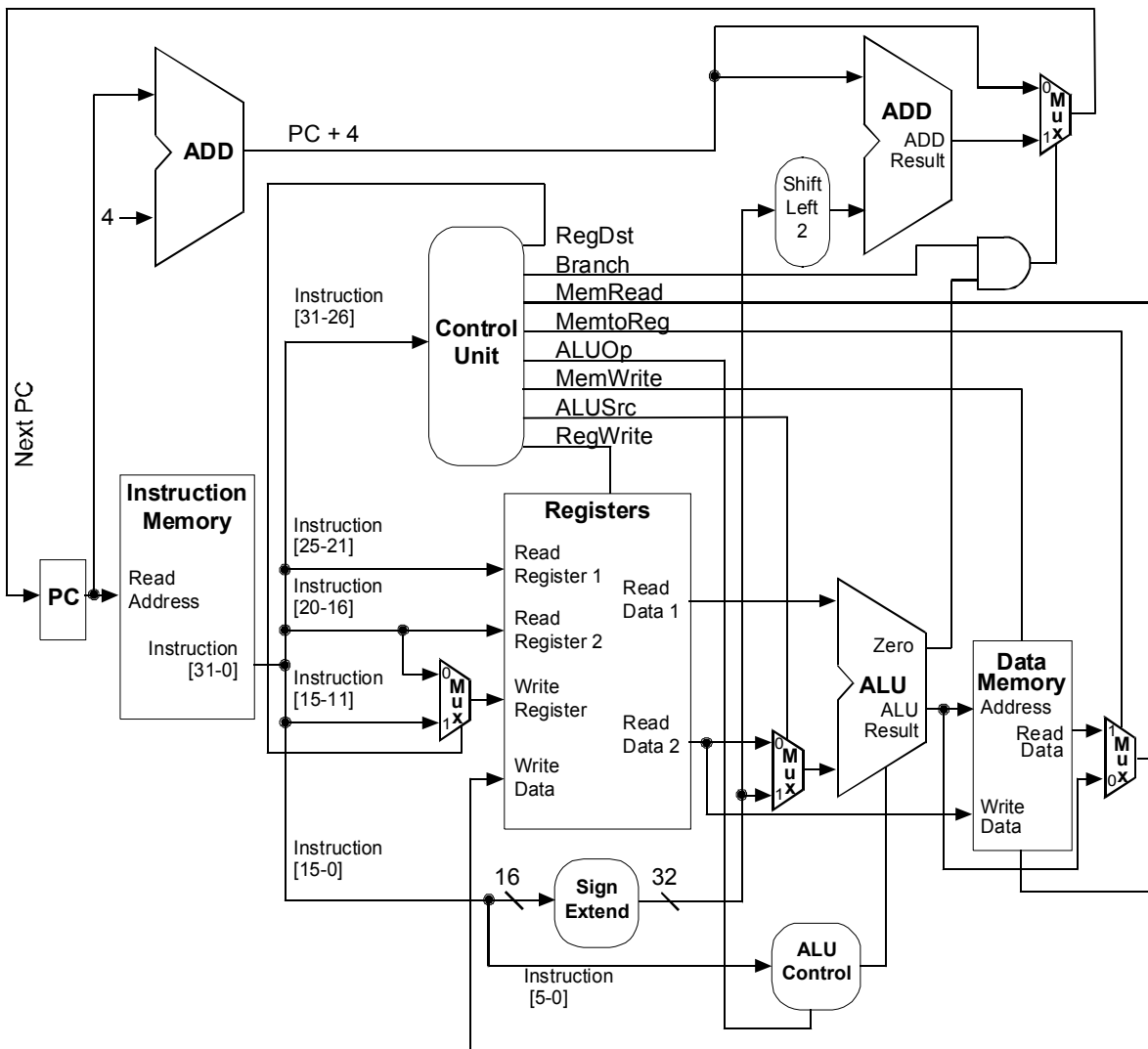


Figure 14.1 MIPS Single Clock Cycle Implementation.

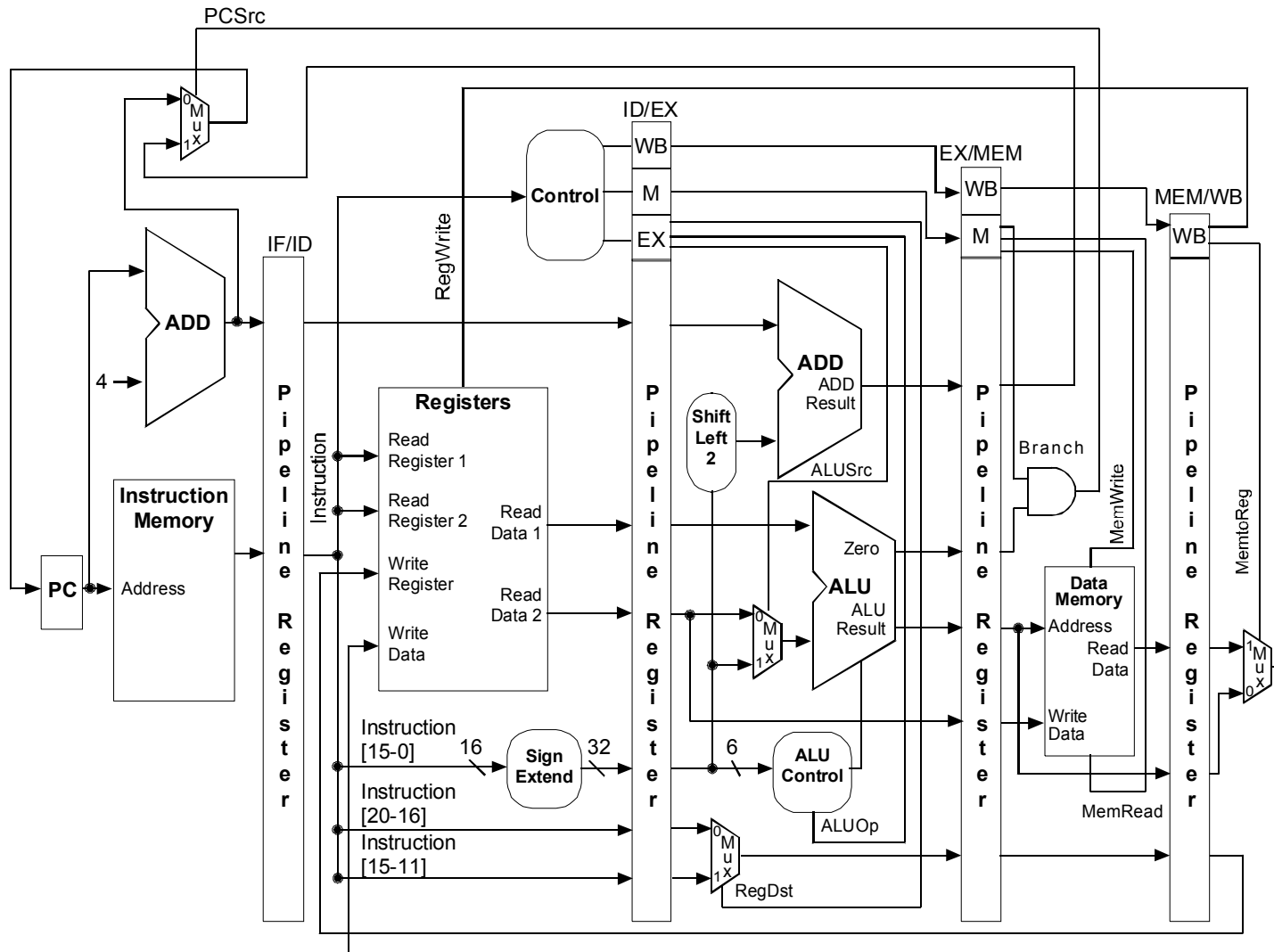


Figure 14.2 MIPS Pipelined Implementation.

-- Top Level Structural Model for MIPS Processor Core

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
USE IEEE.STD_LOGIC_ARITH.ALL;  
ENTITY MIPS IS  
  PORT( reset, clock           : IN STD_LOGIC;  
        -- Output important signals to pins for easy display in Simulator  
        PC                       : OUT STD_LOGIC_VECTOR( 7 DOWNTO 0 );  
        ALU_result_out, read_data_1_out, read_data_2_out,  
        write_data_out, Instruction_out  : OUT STD_LOGIC_VECTOR( 31 DOWNTO 0 );  
        Branch_out, Zero_out, Memwrite_out,  
        Regwrite_out              : OUT  STD_LOGIC );  
END TOP_SPIM;  
ARCHITECTURE structure OF TOP_SPIM IS  
  COMPONENT Ifetch  
    PORT(  Instruction           : OUT STD_LOGIC_VECTOR( 31 DOWNTO 0 );  
          PC_plus_4_out         : OUT  STD_LOGIC_VECTOR( 9 DOWNTO 0 );  
          Add_result            : IN  STD_LOGIC_VECTOR( 7 DOWNTO 0 );  
          Branch                : IN  STD_LOGIC;  
          Zero                  : IN  STD_LOGIC;  
          PC_out                : OUT STD_LOGIC_VECTOR( 9 DOWNTO 0 );  
          clock,reset           : IN  STD_LOGIC );  
END COMPONENT;
```

```

COMPONENT ldecode
  PORT( read_data_1      : OUT  STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        read_data_2      : OUT  STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        Instruction      : IN   STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        read_data       : IN   STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        ALU_result      : IN   STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        RegWrite, MemtoReg : IN  STD_LOGIC;
        RegDst         : IN  STD_LOGIC;
        Sign_extend     : OUT  STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        clock, reset    : IN   STD_LOGIC );

```

END COMPONENT;

```

COMPONENT control
  PORT( Opcode          : IN   STD_LOGIC_VECTOR( 5 DOWNT0 0 );
        RegDst         : OUT  STD_LOGIC;
        ALUSrc         : OUT  STD_LOGIC;
        MemtoReg       : OUT  STD_LOGIC;
        RegWrite       : OUT  STD_LOGIC;
        MemRead        : OUT  STD_LOGIC;
        MemWrite       : OUT  STD_LOGIC;
        Branch         : OUT  STD_LOGIC;
        ALUOp          : OUT  STD_LOGIC_VECTOR( 1 DOWNT0 0 );
        clock, reset   : IN   STD_LOGIC );

```

END COMPONENT;

```

COMPONENT Execute
  PORT( Read_data_1     : IN   STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        Read_data_2     : IN   STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        Sign_Extend     : IN   STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        Function_opcode : IN   STD_LOGIC_VECTOR( 5 DOWNT0 0 );
        ALUOp           : IN   STD_LOGIC_VECTOR( 1 DOWNT0 0 );
        ALUSrc          : IN   STD_LOGIC;
        Zero             : OUT  STD_LOGIC;
        ALU_Result      : OUT  STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        Add_Result      : OUT  STD_LOGIC_VECTOR( 7 DOWNT0 0 );
        PC_plus_4       : IN   STD_LOGIC_VECTOR( 9 DOWNT0 0 );
        clock, reset    : IN   STD_LOGIC );

```

END COMPONENT;

```

COMPONENT dmemory
  PORT( read_data      : OUT  STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        address       : IN   STD_LOGIC_VECTOR( 7 DOWNT0 0 );
        write_data     : IN   STD_LOGIC_VECTOR( 31 DOWNT0 0 );
        MemRead, Memwrite : IN  STD_LOGIC;
        Clock,reset    : IN   STD_LOGIC );

```

END COMPONENT;


```

        -- declare signals used to connect VHDL components
SIGNAL PC_plus_4      : STD_LOGIC_VECTOR( 9 DOWNTO 0 );
SIGNAL read_data_1   : STD_LOGIC_VECTOR( 31 DOWNTO 0 );
SIGNAL read_data_2   : STD_LOGIC_VECTOR( 31 DOWNTO 0 );
SIGNAL Sign_Extend   : STD_LOGIC_VECTOR( 31 DOWNTO 0 );
SIGNAL Add_result    : STD_LOGIC_VECTOR( 7 DOWNTO 0 );
SIGNAL ALU_result    : STD_LOGIC_VECTOR( 31 DOWNTO 0 );
SIGNAL read_data     : STD_LOGIC_VECTOR( 31 DOWNTO 0 );
SIGNAL ALUSrc        : STD_LOGIC;
SIGNAL Branch        : STD_LOGIC;
SIGNAL RegDst        : STD_LOGIC;
SIGNAL Regwrite      : STD_LOGIC;
SIGNAL Zero          : STD_LOGIC;
SIGNAL MemWrite      : STD_LOGIC;
SIGNAL MemtoReg      : STD_LOGIC;
SIGNAL MemRead       : STD_LOGIC;
SIGNAL ALUOp         : STD_LOGIC_VECTOR( 1 DOWNTO 0 );
SIGNAL Instruction   : STD_LOGIC_VECTOR( 31 DOWNTO 0 );

BEGIN

        -- copy important signals to output pins for easy
        -- display in Simulator
Instruction_out <= Instruction;
ALU_result_out    <= ALU_result;
read_data_1_out   <= read_data_1;
read_data_2_out   <= read_data_2;
write_data_out    <= read_data WHEN MemtoReg = '1' ELSE ALU_result;
Branch_out    <= Branch;
Zero_out     <= Zero;
RegWrite_out <= RegWrite;
MemWrite_out <= MemWrite;

```

IFE : Ifetch

```
PORT MAP ( Instruction => Instruction,  
          PC_plus_4_out    => PC_plus_4,  
          Add_result      => Add_result,  
          Branch          => Branch,  
          Zero             => Zero,  
          PC_out          => PC,  
          clock            => clock,  
          reset            => reset );
```

ID : Idecode

```
PORT MAP ( read_data_1 => read_data_1,  
          read_data_2   => read_data_2,  
          Instruction    => Instruction,  
          read_data     => read_data,  
          ALU_result    => ALU_result,  
          RegWrite      => RegWrite,  
          MemtoReg      => MemtoReg,  
          RegDst        => RegDst,  
          Sign_extend   => Sign_extend,  
          clock          => clock,  
          reset          => reset );
```

CTL: control

```
PORT MAP ( Opcode => Instruction( 31 DOWNTO 26 ),  
          RegDst   => RegDst,  
          ALUSrc   => ALUSrc,  
          MemtoReg => MemtoReg,  
          RegWrite => RegWrite,  
          MemRead  => MemRead,  
          MemWrite => MemWrite,  
          Branch   => Branch,  
          ALUOp    => ALUOp,  
          clock    => clock,  
          reset    => reset );
```

EXE: Execute

```
PORT MAP ( Read_data_1 => read_data_1,  
          Read_data_2   => read_data_2,  
          Sign_extend   => Sign_extend,  
          Function_opcode => Instruction( 5 DOWNTO 0 ),  
          ALUOp         => ALUOp,  
          ALUSrc        => ALUSrc,  
          Zero          => Zero,  
          ALU_Result    => ALU_Result,  
          Add_Result    => Add_Result,  
          PC_plus_4     => PC_plus_4,  
          Clock         => clock,  
          Reset         => reset );
```

MEM: dmemory

```
PORT MAP ( read_data => read_data,  
          address    => ALU_Result,  
          write_data => read_data_2,  
          MemRead    => MemRead,  
          Memwrite   => MemWrite,  
          clock      => clock,  
          reset      => reset );
```

END structure;

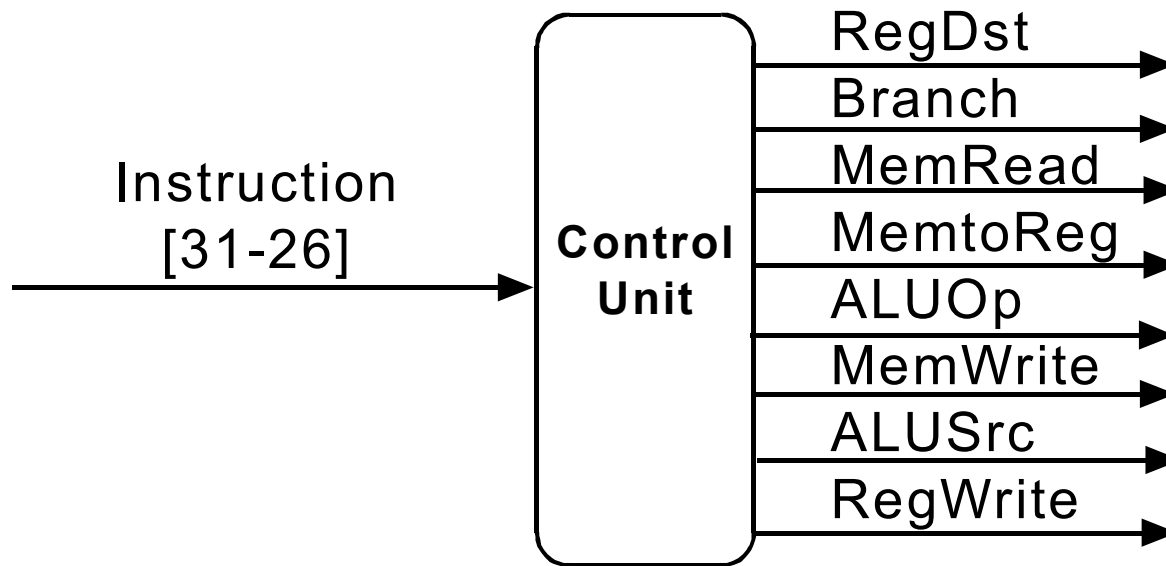


Figure 14.3 Block Diagram of MIPS Control Unit

-- control module (implements MIPS control unit)

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_SIGNED.ALL;
ENTITY control IS
    PORT( Opcode          : IN   STD_LOGIC_VECTOR( 5 DOWNTO 0 );
          RegDst         : OUT  STD_LOGIC;
          ALUSrc         : OUT  STD_LOGIC;
          MemtoReg       : OUT  STD_LOGIC;
          RegWrite       : OUT  STD_LOGIC;
          MemRead        : OUT  STD_LOGIC;
          MemWrite       : OUT  STD_LOGIC;
          Branch         : OUT  STD_LOGIC;
          ALUOp          : OUT  STD_LOGIC_VECTOR( 1 DOWNTO 0 );
          clock, reset   : IN   STD_LOGIC );
```

END control;

ARCHITECTURE behavior OF control IS

```
    SIGNAL R_format, Lw, Sw, Beq : STD_LOGIC;
```

BEGIN

-- Code to generate control signals using opcode bits

```
    R_format <= '1' WHEN Opcode = "000000" ELSE '0';
    Lw       <= '1' WHEN Opcode = "100011" ELSE '0';
    Sw       <= '1' WHEN Opcode = "101011" ELSE '0';
    Beq      <= '1' WHEN Opcode = "000100" ELSE '0';
    RegDst   <= R_format;
    ALUSrc   <= Lw OR Sw;
    MemtoReg <= Lw;
    RegWrite <= R_format OR Lw;
    MemRead  <= Lw;
    MemWrite <= Sw;
    Branch   <= Beq;
    ALUOp( 1 ) <= R_format;
    ALUOp( 0 ) <= Beq;
```

END behavior;

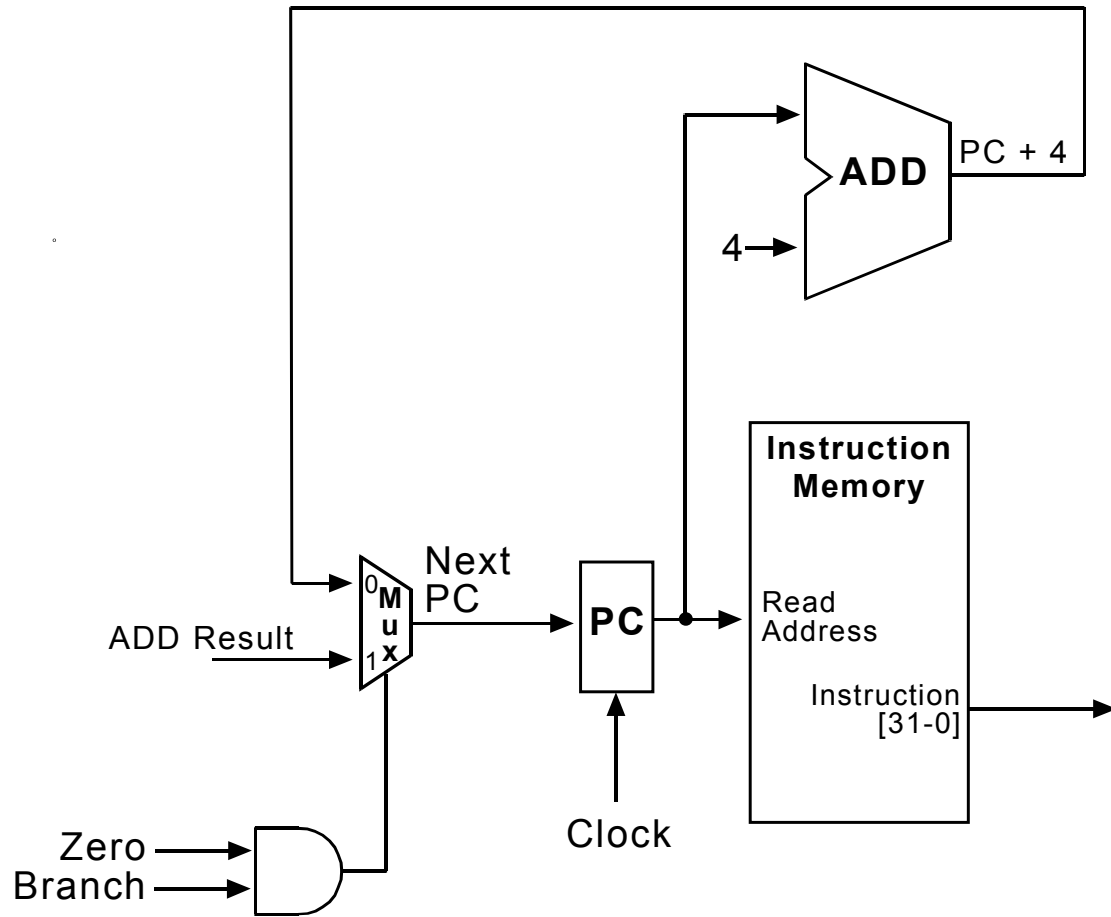


Figure 14.4 Block Diagram of MIPS Fetch Unit.

```

-- Ifetch module (provides the PC and instruction
--memory for the MIPS computer)
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
LIBRARY altera_mf;
USE altera_mf.altera_mf_components.ALL;
ENTITY Ifetch IS
    PORT(
        SIGNAL Instruction : OUT    STD_LOGIC_VECTOR( 31 DOWNTO 0 );
        SIGNAL PC_plus_4_out : OUT    STD_LOGIC_VECTOR( 7 DOWNTO 0 );
        SIGNAL Add_result : IN    STD_LOGIC_VECTOR( 7 DOWNTO 0 );
        SIGNAL Branch : IN    STD_LOGIC;
        SIGNAL Zero : IN    STD_LOGIC;
        SIGNAL PC_out : OUT STD_LOGIC_VECTOR( 9 DOWNTO 0 );
        SIGNAL clock, reset : IN    STD_LOGIC);
END Ifetch;
ARCHITECTURE behavior OF Ifetch IS
    SIGNAL PC, PC_plus_4 : STD_LOGIC_VECTOR( 9 DOWNTO 0 );
    SIGNAL next_PC : STD_LOGIC_VECTOR( 7 DOWNTO 0 );
BEGIN
    --ROM for Instruction Memory
    data_memory: altsyncram

    GENERIC MAP (
        operation_mode => "ROM",
        width_a => 32,
        widthad_a => 8,
        lpm_type => "altsyncram",
        outdata_reg_a => "UNREGISTERED",
        -- Reads in mif file for initial data memory values
        init_file => "program.mif",
        intended_device_family => "Cyclone")
    PORT MAP (
        clock0 => clock,
        address_a => Mem_Addr,
        q_a => Instruction
    );

```

```

PC(1 DOWNTO 0) <= "00";
-- Instructions always start on a word address - not byte

PC_out          <= PC;
PC_plus_4_out   <= PC_plus_4;
-- copy output signals - allows read inside module

Mem_Addr <= Next_PC;
-- send word address to inst. memory address register

PC_plus_4( 9 DOWNTO 2 ) <= PC( 9 DOWNTO 2 ) + 1;
PC_plus_4( 1 DOWNTO 0 ) <= "00";
-- Adder to increment PC by 4
-- Mux to select Branch Address or PC + 4

Next_PC <= X"00" WHEN Reset = '1' ELSE
  Add_result WHEN ( ( Branch = '1' ) AND ( Zero = '1' ) )
  ELSE PC_plus_4( 9 DOWNTO 2 );
-- Store PC in register and load next PC on clock edge

PROCESS
BEGIN
  WAIT UNTIL ( clock'EVENT ) AND ( clock = '1' );
  IF reset = '1' THEN
    PC <= "0000000000" ;
  ELSE
    PC( 9 DOWNTO 2 ) <= Next_PC;
  END IF;
END PROCESS;
END behavior;

```

```

-- MIPS Instruction Memory Initialization File
Depth = 256;
Width = 32;
Address_radix = HEX;
Data_radix = HEX;
Content
Begin
    -- Use NOPS for default instruction memory values
    [00..FF]: 00000000;      -- nop (sll r0,r0,0)
    -- Place MIPS Instructions here
    -- Note: memory addresses are in words and not bytes
    -- i.e. next location is +1 and not +4

    00: 8C020000;      -- lw $2,0 ;memory(00)=55
    01: 8C030001;      -- lw $3,1 ;memory(01)=AA
    02: 00430820;      -- add $1,$2,$3
    03: AC010003;      -- sw $1,3 ;memory(03)=FF
    04: 1022FFFF;      -- beq $1,$2,-4
    05: 1021FFFA;      -- beq $1,$1,-24

End;

```

Figure 14.5 MIPS Program Memory Initialization File, program.mif.

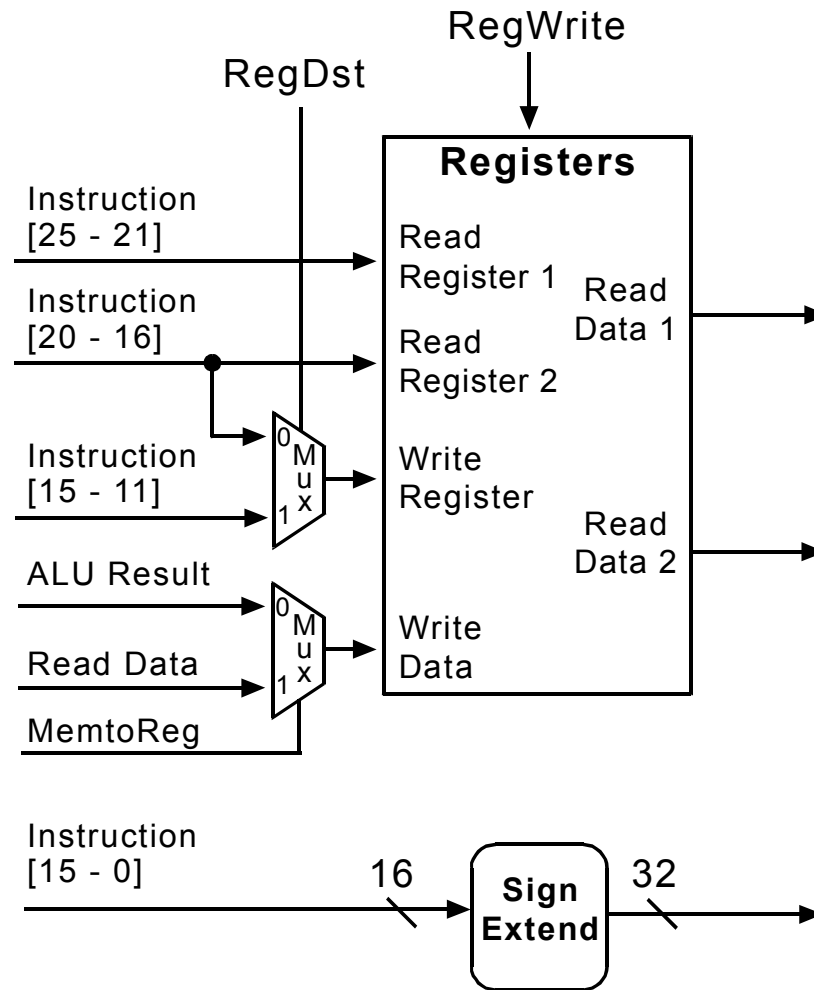


Figure 14.6 Block Diagram of MIPS Decode Unit.

```

-- Idecode module (implements the register file for
LIBRARY IEEE;           -- the MIPS computer)
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
ENTITY Idecode IS
    PORT( read_data_1    : OUT STD_LOGIC_VECTOR( 31 DOWNTO 0 );
          read_data_2  : OUT STD_LOGIC_VECTOR( 31 DOWNTO 0 );
          Instruction    : IN  STD_LOGIC_VECTOR( 31 DOWNTO 0 );
          read_data     : IN  STD_LOGIC_VECTOR( 31 DOWNTO 0 );
          ALU_result    : IN  STD_LOGIC_VECTOR( 31 DOWNTO 0 );
          RegWrite      : IN  STD_LOGIC;
          MemtoReg      : IN  STD_LOGIC;
          RegDst         : IN  STD_LOGIC;
          Sign_extend   : OUT STD_LOGIC_VECTOR( 31 DOWNTO 0 );
          clock,reset   : IN  STD_LOGIC );
END Idecode;
ARCHITECTURE behavior OF Idecode IS
TYPE register_file IS ARRAY ( 0 TO 31 ) OF STD_LOGIC_VECTOR( 31 DOWNTO 0 );
SIGNAL register_array: register_file;
SIGNAL write_register_address : STD_LOGIC_VECTOR( 4 DOWNTO 0 );
SIGNAL write_data             : STD_LOGIC_VECTOR( 31 DOWNTO 0 );
SIGNAL read_register_1_address : STD_LOGIC_VECTOR( 4 DOWNTO 0 );
SIGNAL read_register_2_address : STD_LOGIC_VECTOR( 4 DOWNTO 0 );
SIGNAL write_register_address_1 : STD_LOGIC_VECTOR( 4 DOWNTO 0 );
SIGNAL write_register_address_0 : STD_LOGIC_VECTOR( 4 DOWNTO 0 );
SIGNAL Instruction_immediate_value : STD_LOGIC_VECTOR( 15 DOWNTO 0 );

```

BEGIN

```
read_register_1_address    <= Instruction( 25 DOWNTO 21 );
read_register_2_address    <= Instruction( 20 DOWNTO 16 );
write_register_address_1    <= Instruction( 15 DOWNTO 11 );
write_register_address_0    <= Instruction( 20 DOWNTO 16 );
Instruction_immediate_value <= Instruction( 15 DOWNTO 0 );
                           -- Read Register 1 Operation
read_data_1 <= register_array( CONV_INTEGER( read_register_1_address ) );
                           -- Read Register 2 Operation
read_data_2 <= register_array( CONV_INTEGER( read_register_2_address ) );
                           -- Mux for Register Write Address
write_register_address <= write_register_address_1
                           WHEN RegDst = '1' ELSE write_register_address_0;
                           -- Mux to bypass data memory for Rformat instructions
write_data <= ALU_result( 31 DOWNTO 0 )
                           WHEN ( MemtoReg = '0' ) ELSE read_data;
                           -- Sign Extend 16-bits to 32-bits
Sign_extend <= X"0000" & Instruction_immediate_value
                           WHEN Instruction_immediate_value(15) = '0'
                           ELSE  X"FFFF" & Instruction_immediate_value;
```

PROCESS

BEGIN

```
WAIT UNTIL clock'EVENT AND clock = '1';
```

```
IF reset = '1' THEN
```

```
                           -- Initial register values on reset are register = reg#
                           -- use loop to automatically generate reset logic
                           -- for all registers
```

```
FOR i IN 0 TO 31 LOOP
```

```
    register_array(i) <= CONV_STD_LOGIC_VECTOR( i, 32 );
```

```
END LOOP;
```

```
                           -- Write back to register - don't write to register 0
```

```
ELSIF RegWrite = '1' AND write_register_address /= 0 THEN
```

```
    register_array( CONV_INTEGER( write_register_address )) <= write_data;
```

```
END IF;
```

```
END PROCESS;
```

```
END behavior;
```

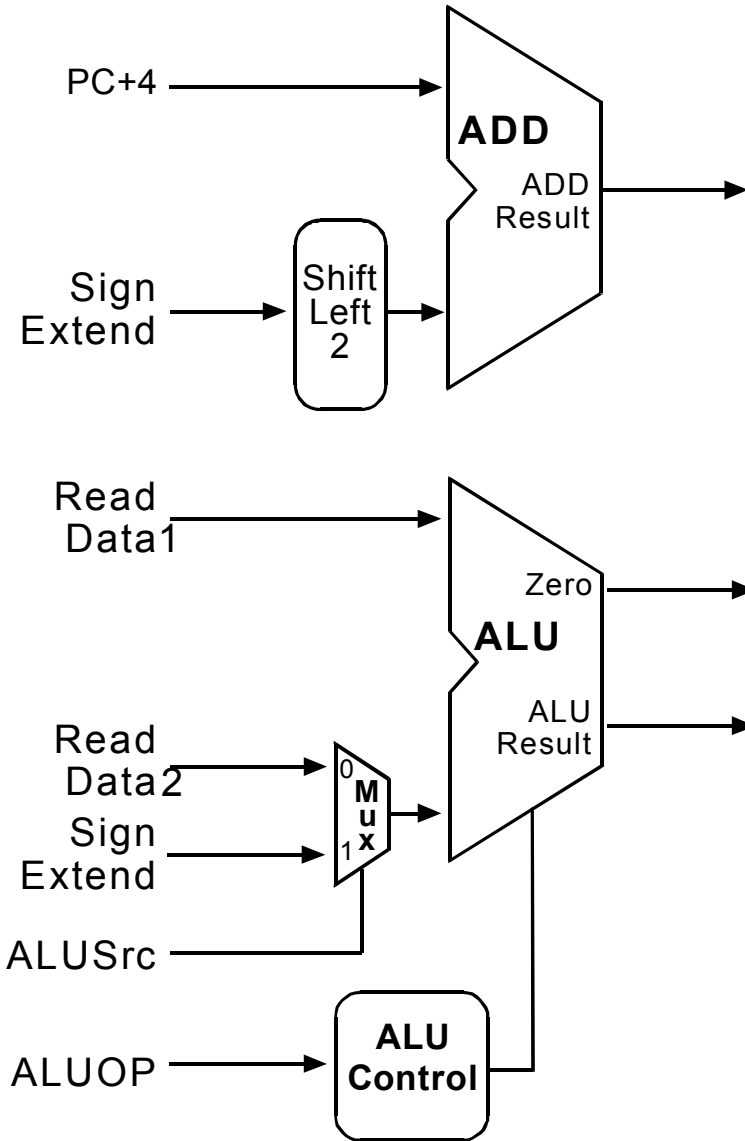


Figure 13.7 Block Diagram of MIPS Execute Unit.

*-- Execute module (implements the data ALU and Branch Address Adder
-- for the MIPS computer)*

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_ARITH.ALL;

USE IEEE.STD_LOGIC_SIGNED.ALL;

ENTITY Execute IS

PORT(Read_data_1 : IN STD_LOGIC_VECTOR(31 DOWNT0 0);

Read_data_2 : IN STD_LOGIC_VECTOR(31 DOWNT0 0);

Sign_extend : IN STD_LOGIC_VECTOR(31 DOWNT0 0);

Function_opcode : IN STD_LOGIC_VECTOR(5 DOWNT0 0);

ALUOp : IN STD_LOGIC_VECTOR(1 DOWNT0 0);

ALUSrc : IN STD_LOGIC;

Zero : OUT STD_LOGIC;

ALU_Result : OUT STD_LOGIC_VECTOR(31 DOWNT0 0);

Add_Result : OUT STD_LOGIC_VECTOR(7 DOWNT0 0);

PC_plus_4 : IN STD_LOGIC_VECTOR(7 DOWNT0 0);

clock, reset : IN STD_LOGIC);

END Execute;

ARCHITECTURE behavior OF Execute IS

SIGNAL Ainput, Binput : STD_LOGIC_VECTOR(31 DOWNT0 0);

SIGNAL ALU_output_mux : STD_LOGIC_VECTOR(31 DOWNT0 0);

SIGNAL Branch_Add : STD_LOGIC_VECTOR(8 DOWNT0 0);

SIGNAL ALU_ctl : STD_LOGIC_VECTOR(2 DOWNT0 0);

```

BEGIN
    Ainput <= Read_data_1;
        -- ALU input mux
    Binput <= Read_data_2
    WHEN ( ALUSrc = '0' )
    ELSE Sign_extend( 31 DOWNT0 0 );
        -- Generate ALU control bits
    ALU_ctl( 0 ) <= ( Function_opcode( 0 ) OR Function_opcode( 3 ) ) AND ALUOp(1);
    ALU_ctl( 1 ) <= ( NOT Function_opcode( 2 ) ) OR (NOT ALUOp( 1 ) );
    ALU_ctl( 2 ) <= ( Function_opcode( 1 ) AND ALUOp( 1 ) ) OR ALUOp( 0 );
        -- Generate Zero Flag

    Zero <= '1'
    WHEN ( ALU_output_mux( 31 DOWNT0 0 ) = X"00000000" )
    ELSE '0';
        -- Select ALU output for SLT

    ALU_result <= X"00000000" & B"000" & ALU_output_mux( 31 )
    WHEN ALU_ctl = "111"
    ELSE ALU_output_mux( 31 DOWNT0 0 );
        -- Adder to compute Branch Address

    Branch_Add <= PC_plus_4( 9 DOWNT0 2 ) + Sign_extend( 7 DOWNT0 0 );
    Add_result <= Branch_Add( 7 DOWNT0 0 );
PROCESS ( ALU_ctl, Ainput, Binput )
BEGIN
    -- Select ALU operation
CASE ALU_ctl IS
    -- ALU performs ALUresult = A_input AND B_input
    WHEN "000" => ALU_output_mux <= Ainput AND Binput;
    -- ALU performs ALUresult = A_input OR B_input
    WHEN "001" => ALU_output_mux <= Ainput OR Binput;
    -- ALU performs ALUresult = A_input + B_input
    WHEN "010" => ALU_output_mux <= Ainput + Binput;
    -- ALU performs ?
    WHEN "011" => ALU_output_mux <= X"00000000" ;
    -- ALU performs ?
    WHEN "100" => ALU_output_mux <= X"00000000" ;
    -- ALU performs ?
    WHEN "101" => ALU_output_mux <= X"00000000" ;
    -- ALU performs ALUresult = A_input - B_input
    WHEN "110" => ALU_output_mux <= Ainput - Binput;
    -- ALU performs SLT
    WHEN "111" => ALU_output_mux <= Ainput - Binput ;
    WHEN OTHERS => ALU_output_mux <= X"00000000" ;
END CASE;
END PROCESS;
END behavior;

```

 


Figure 14.8 Block Diagram of MIPS Data Memory Unit.

```

-- Dmemory module (implements the data
-- memory for the MIPS computer)
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_SIGNED.ALL;
LIBRARY altera_mf;
USE altera_mf.altera_mf_components.ALL;
ENTITY dmemory IS
    PORT(
        read_data          : OUT    STD_LOGIC_VECTOR( 31 DOWNTO 0 );
        address             : IN     STD_LOGIC_VECTOR( 7 DOWNTO 0 );
        write_data          : IN     STD_LOGIC_VECTOR( 31 DOWNTO 0 );
        MemRead, Memwrite  : IN     STD_LOGIC;
        clock, reset       : IN     STD_LOGIC );
END dmemory;
ARCHITECTURE behavior OF dmemory IS
    SIGNAL write_clock : STD_LOGIC;
BEGIN

    data_memory: altsyncram
    GENERIC MAP (
        operation_mode => "SINGLE_PORT",
        width_a => 32,
        widthad_a => 8,
        lpm_type => "altsyncram",
        outdata_reg_a => "UNREGISTERED",
        -- Reads in mif file for initial data memory values
        init_file => "dmemory.mif",
        intended_device_family => "Cyclone"lpm_widthad    =>      8
    )
    PORT MAP (
        wren_a => memwrite,
        clock0 => write_clock,
        address_a => address,
        data_a => write_data,
        q_a => read_data );
        -- Load memory address & data register with write clock
        write_clock <= NOT clock;
END behavior;

```



```
-- MIPS Data Memory Initialization File
Depth = 256;
Width = 32;
Content
Begin
  -- default value for memory
  [00..FF] : 00000000;
  -- initial values for test program
  00 : 55555555;
  01 : AAAAAAAAAA;
End;
```

Figure 14.9 MIPS Data Memory Initialization File, dmemory.mif.

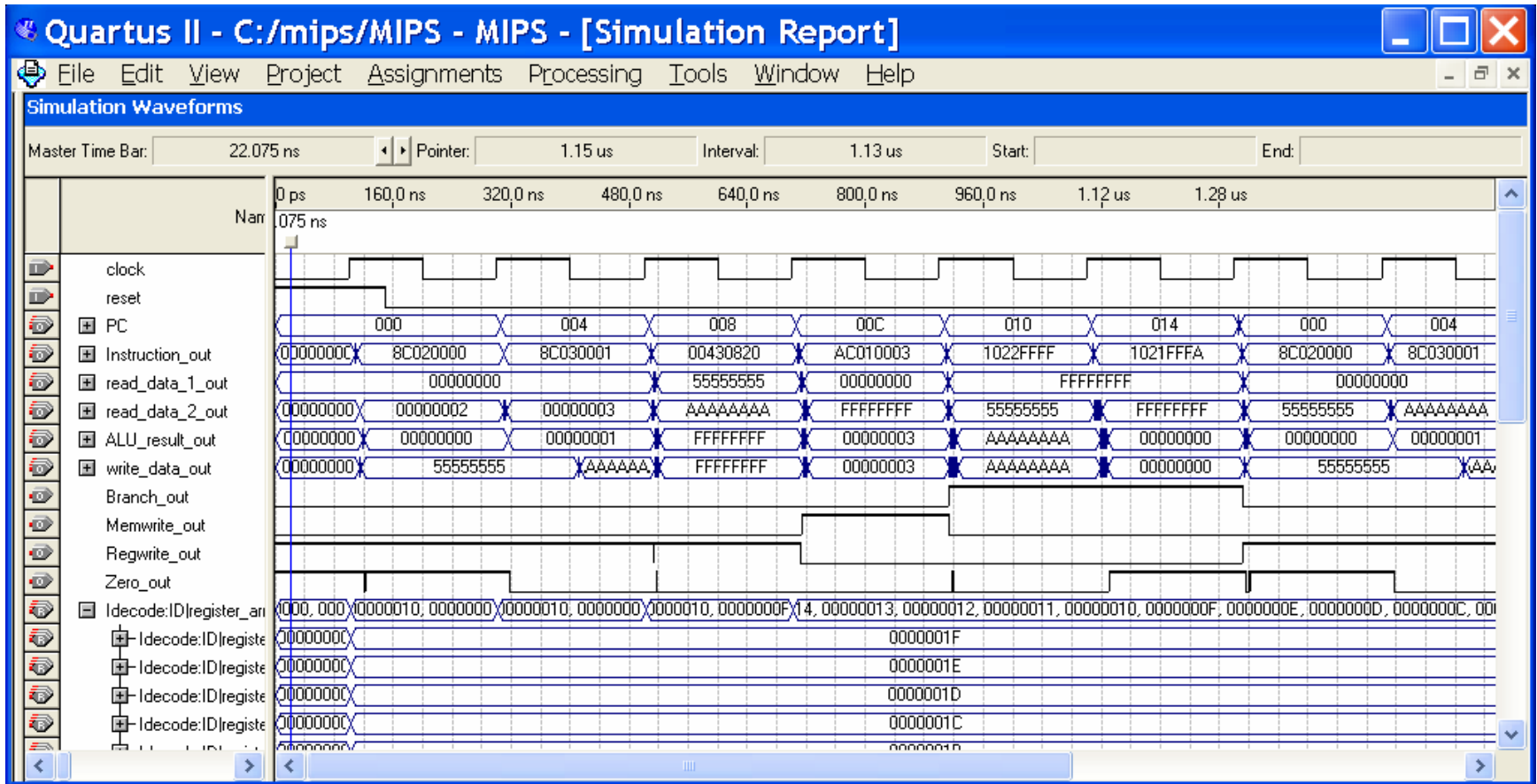


Figure 14.10 Simulation of MIPS test program.

| MIPS | COMPUTER |
|------|----------|
| PC | 00000008 |
| INST | 00430820 |
| REG1 | 00000055 |
| REG2 | 000000AA |
| ALU | 000000FF |
| W.B. | 000000FF |
| BRAN | 0 |
| ZERO | 0 |
| MEMR | 0 |
| MEMW | 0 |
| CLK | + |
| RST | + |

Figure 14.11 MIPS with Video Output generated by UP 1 Board.